

CS E231

Assignment 04

MD Mostafijur Rahman

ID: 22101721

Section: 14

Q1

The method of assumed state is used to analyze mosfet circuit because mosfets operate in different regions (cutoff, triode, saturation).

This method involves assuming the mosfets operating region solving the circuit based on that assumption and then verifying if the solution aligns with assumed region. If the assumption is incorrect then we assume new region and the process repeat.

Question 2

a. Given that, get current $I_G = 0$

$$I_{DS} = 4 \text{ mA}$$

$V_G = \text{Ground connected SO if } V_{GS} = 0$

b.

$$\partial_{DS} = \frac{5 - V_D}{1}$$

$$\Rightarrow 4 = 5 - V_D$$

$$V_D = 1 \text{ V}$$

Ans

Ans

Assume 'saturation' or $v_{ds} = 0$

$$V_{DS} = V_D - V_S$$

$$= 0 - x$$

$$V_{DS} = -x$$

$$V_T = 1$$

$$V_{DS} = V_{DS} - V_T$$

$$= -x - 1$$

$$= -(x+1)$$

$$I_{DS} = \frac{12}{2} V_{DS}^2$$

$$\Rightarrow 4 = \frac{4}{2} (x+1)^2$$

$$\Rightarrow 2 = (x+1)^2$$

$$\Rightarrow x^2 + 2x - 1 = 0$$

Solving eq,

$$x_1 = 0.4142$$

$$x_2 = -2.4142$$

$$x_1 = 0.4142$$

$$V_{DS} = V_D - V_S$$

$$= 1 - x$$

$$= 1 - 0.4142 = 0.5864$$

$$\approx 0.6$$

$$V_{DS} = -4.414 \text{ V}$$

V_{DS} negative $\therefore V_{DS} < V_T$ so mostet off


$$x = -2.4142$$

$$V_{OV} = -1.414V$$

$$V_{DS} = 3.414V$$

$V_{DS} > V_{OV}$ γ_{D0} assumption is right its saturation voltage.

Question 3

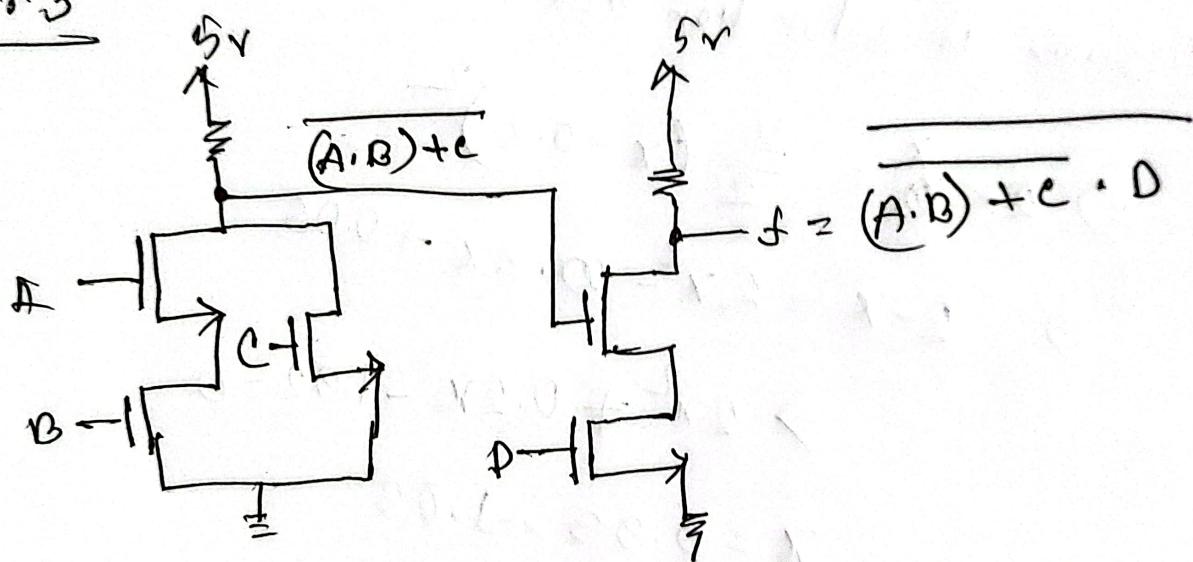

Question 4

$$V_{DS} \neq V_G - V_S$$

$$= V_G - 0 = V_G = x$$

$$V_{DS} = V_D - V_S = V_D = V_G = x \quad (V_G = V_D)$$

$$V_{DS} = V_{GS} - V_T = V_G - 0.2 = x - 0.2$$

Assume it saturation mode

$$\Rightarrow 2 - x = \frac{k}{2} (x - 0.2)^2$$

$$\Rightarrow 2 - x = 2x^2 - 0.8x + 0.08$$

$$\Rightarrow 2x^2 + 0.2x - 1.92 = 0$$

$$x = 0.93, -1.03$$

?

when

$$V_D = 0.93, 0.2 = 0.73$$

$$V_D = 0.93$$

$$I_D = 1.06 \text{ mA} \quad V_{GS} > V_T$$

$V_D = -1.03$
 $V_{GS} > V_T$
 (mosfet
turn on)
 $I_D \neq 3.03 \text{ mA}$

$$V_D = 0.93 \text{ V and } I_D = 1.06 \text{ mA}$$

Question 5

